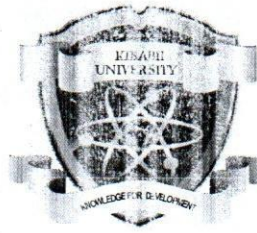


68



*(Knowledge for Development)*

**KIBABII UNIVERSITY  
UNIVERSITY EXAMINATIONS  
2020/2021 ACADEMIC YEAR**

**END OF SEMESTER EXAMINATIONS  
YEAR ONE SEMESTER ONE EXAMINATIONS  
(JAN INTAKE)**

**FOR THE DEGREE OF  
BACHELOR OF SCIENCE  
(COMPUTER SCIENCE)**

**COURSE CODE : CSC 116  
COURSE TITLE : ELECTRICAL  
PRINCIPLES**


**DATE: WEDNESDAY 12<sup>TH</sup>, MAY 2021 TIME: 2.00 P.M -4.00 P.M**

**INSTRUCTIONS TO CANDIDATES**

**ANSWER QUESTIONS ONE AND ANY OTHER TWO.**


**QUESTION ONE [COMPULSORY] [30 MARKS]**

- a) Calculate the resistance of a copper cable with length 3200 meters and cross section  $240 \text{ mm}^2$  [3 marks]
- b) Calculate the resistance of the heating element in a toaster rated at 1.2kw, 240V.[3marks]
- c) Determine the current rating of a fuse whose resistance is 1 ohm and a maximum power rating of 0.25W. [2 marks]
- d) For the circuit of figure 1, Calculate
  - i) The equivalent resistance [3 marks]
  - ii) The supply voltage V in the circuit shown. [6 marks]

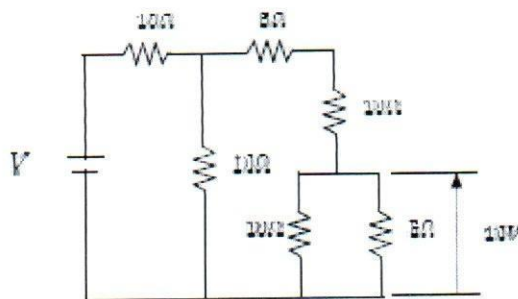

**Figure 1**

- e) The terminal voltage of an open current source is 450V and its short circuit current is 18A. Calculate the internal resistance of the source. [2 marks]
- f) Determine the voltage  $v_3$  in the circuit of Figure 2, given that  $R_1 = 10\Omega$ ;  $R_2 = 6\Omega$ ;  $R_3 = 8\Omega$  and  $V_S = 3 \text{ V}$ .

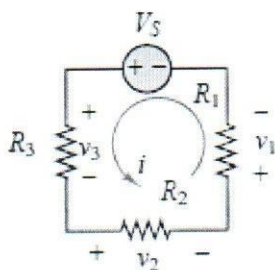

**Figure 2**

- g) Given that the charge stored by a capacitor is  $5 \mu\text{C}$  and is charged to 50 V, find its capacitance. [2 marks]

- h) Three resistors  $R_1$ ,  $R_2$  and  $R_3$  are connected in series to a 240V dc source. The combined voltage drop across  $R_1$  and  $R_2$  is 165V. The combined voltage drop across  $R_2$  and  $R_3$  is 180V. If the total resistance is 8000 ohms, calculate the resistance of each of the three resistors. [6 marks]
- i) Three lamps operating in parallel on a 240V line are rated at 30W, 40W and 50W respectively. Determine the equivalent resistance of this load. [3 marks]

**QUESTION TWO [20 MARKS]**

- a) Three resistors connected in parallel draw a total of 20mA from the source. If the resistor values are  $8k\Omega$ ,  $20k\Omega$  and  $40k\Omega$  respectively, calculate the current flowing through each resistor [5 marks]
- b) Using the circuit of figure 3, calculate:
- The equivalent resistance of the network when the load current is zero [5 marks]
  - The input voltage when the load current is 10mA. [2 marks]

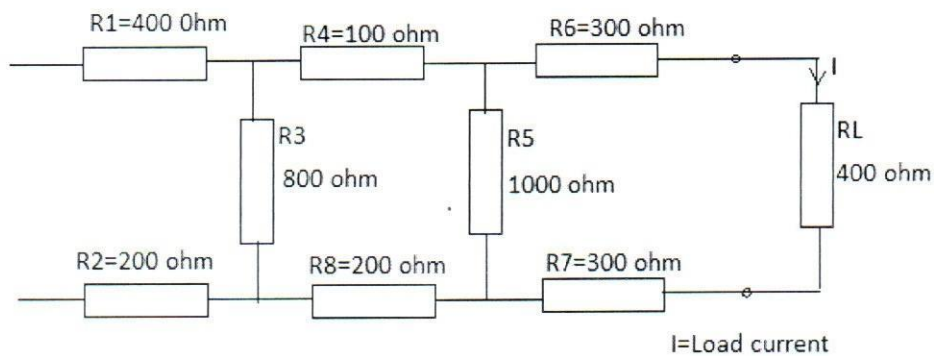


Figure 3

- c) Find the mesh currents in the circuit of Figure 4 [8 marks]



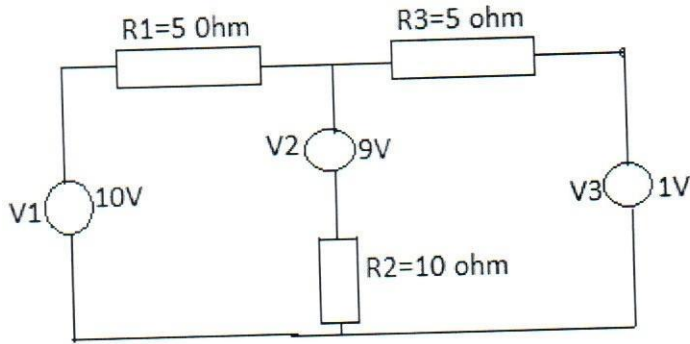


Figure 4

- d) Three capacitors A, B, C have capacitances 10, 50 and 25  $\mu\text{F}$  respectively. Calculate:
- Charge on each capacitor when connected in parallel to a 250V supply. [2marks]
  - The total capacitance [1 mark]
  - P,d across each when connected in series. [2 marks]

**QUESTION THREE [20 MARKS]**

- a) In a given R-L circuit,  $R=3.5\Omega$  and  $L=0.1\text{H}$ . find
- The current through the circuit [3 marks]
  - The power factor if a 50-Hz voltage  $V=250\angle 30^\circ$  is applied across the circuit. [5 marks]
- b) A resistance of 20 ohms, inductance of 0.2H and a capacitance of 150 $\mu\text{F}$  are connected in series across 230V, 50Hz supply. Find:
- $X_L$
  - $X_C$
  - $Z$
  - power factor
  - Active power
  - Reactive power
- [12 marks]

**QUESTION FOUR [20 MARKS]**

- a) Using Kirchhoff's laws, calculate the current in each branch of the network of Figure 5 [10 marks]  
below:

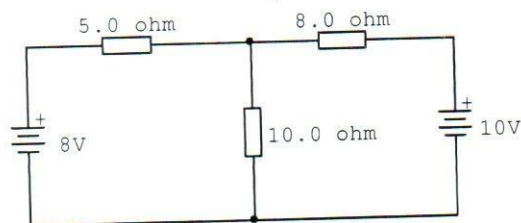


Figure 5

b) A parallel circuit consists of a 200-ohm resistor, an inductance of reactance 100 ohm and a capacitor of reactance 80 ohm across 120V ac source. Determine:

ii) The branch currents

iii) The total current

iv) The impedance

[10 marks]

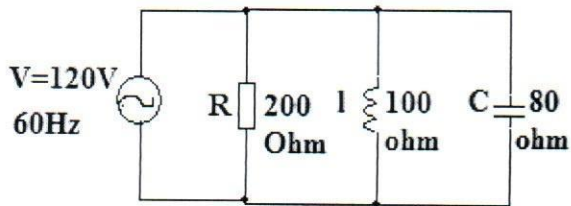


Figure 6

**QUESTION FIVE [20 MARKS]**

a) Using node voltage method, find the current through the 3-ohm resistor for the network shown in Figure 7. [8 marks]

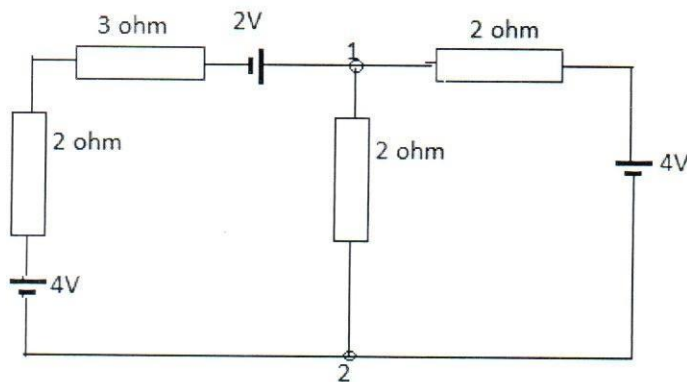


Figure 7

b) Find and solve the node equations of the network of Figure 8. Hence find the power consumed by the passive elements of the network. [12 marks]

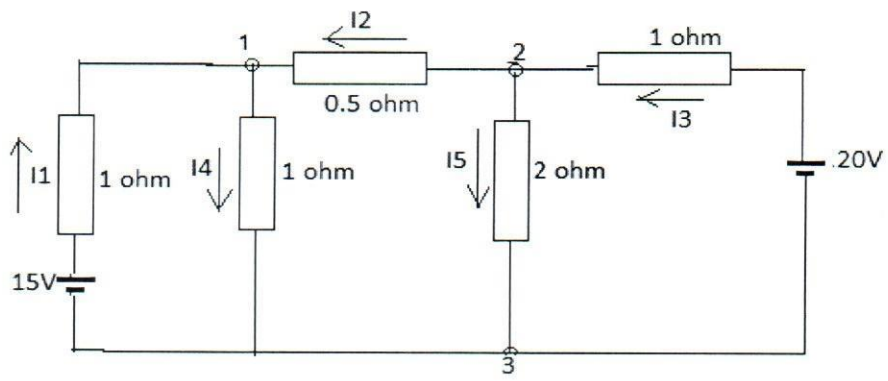


Figure 8