

38



# **KIBABII UNIVERSITY**

**UNIVERSITY EXAMINATIONS  
2020/2021 ACADEMIC YEAR**

**SECOND YEAR FIRST SEMESTER  
MAIN EXAMINATIONS**

**FOR THE DEGREE OF B.SC (RENEWABLE ENERGY AND BIOFUELS  
TECHNOLOGY)**

**COURSE CODE: REN 213**

**COURSE TITLE: BASIC ELECTRONICS TECHNOLOGY**

**DATE: 21/06/2021**

**TIME: 2-4PM**

---

## **INSTRUCTIONS TO CANDIDATES**

TIME: 2 Hours

**Answer question ONE and any TWO of the remaining**

KIBU observes ZERO tolerance to examination cheating

### Question One (Compulsory)

- a) Name four types of diodes. (2 marks)
- b) Define the term rectification. (2 marks)
- c) List three main properties of an op amp. (3 marks)
- d) Define the cut-off frequency for a filter. (2 marks)
- e) Differentiate between a band-pass filter and band-stop filter. (4 marks)
- f) Determine the decimal equivalent of  $11001_2$ . (3 marks)
- g) State four types of logic gates. (4 marks)
- h) State DE Morgan's theorem. (4 marks)
- i) Define the term 'flip flop' (2 marks)
- j) Define the following terms as applied in computer systems: (4 marks)
  - i. Microprocessor
  - ii. Software

### Question Two

- a) With the aid of diagrams explain the formation of N and P type semiconductors. (10 marks)
- b) State four types of logic families. (4 marks)
- c) Figure 1 below shows a three input OR gate. Draw its truth table. (6 marks)

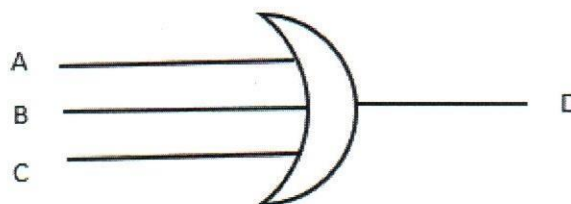


Figure 1

### Question Three

- a) For the summing op-amp shown in figure 2, determine the output voltage,  $V_0$ . (10 marks)

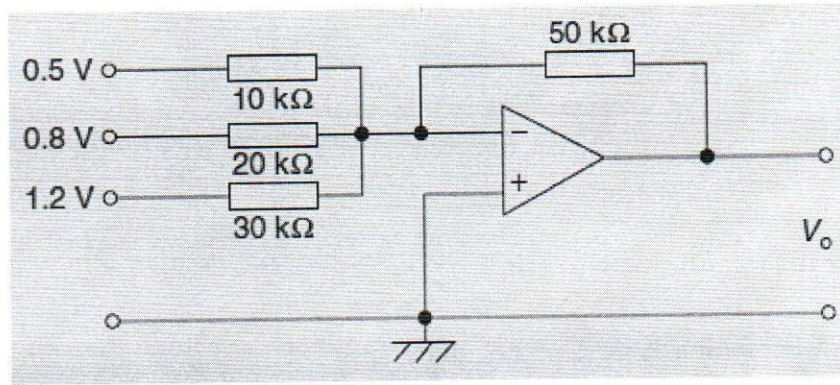


Figure 2

- b) With aid of a diagram, describe the operation of a NPN bipolar junction transistor. (10 marks)

**Question Four**

- a) Draw a labelled diagram of the general microprocessor architecture of an intel 8085. (20 marks)

**Question Five**

- a) Highlight five applications of logic gates. (5 marks)
- b) Differentiate between a combinational logic circuit and a sequential logic circuit. (4 marks)
- c) Determine the cut-off frequency and the nominal impedance for the low-pass T-connected section shown in figure 3. (11 marks)

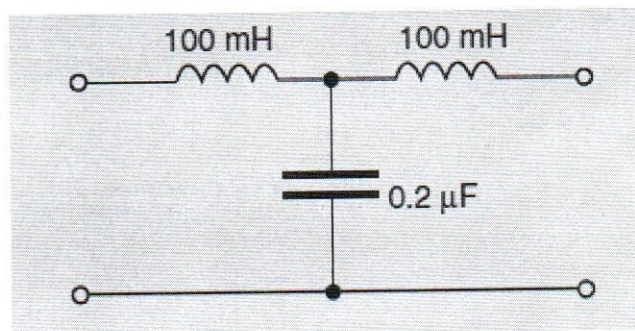


Figure 3