



*(Knowledge for Development)*

**KIBABII UNIVERSITY**

**(KIBU)**

**UNIVERSITY EXAMINATIONS  
2019/2020 ACADEMIC YEAR**

**SPECIAL/SUPPLEMENTARY EXAMINATION  
YEAR TWO SEMESTER TWO**

**FOR THE DIPLOMA  
INFORMATION TECHNOLOGY**

**COURSE CODE : DIT 079**

**COURSE TITLE : DIGITAL ELECTRONICS**

**DATE: 17/02/2021**

**TIME: 2.00 P.M – 4.00 P.M.**

**INSTRUCTIONS**

**ANSWER QUESTIONS ONE AND ANY OTHER TWO.**

**QUESTION ONE (COMPULSORY) [24 MARKS]**

- a) Categorize the different ways of representing numerical values of quantities. [2 marks]
- b) Define the term digital quantity hence state an example. [3 marks]
- c) Name the different number systems used in digital technology. [4 marks]
- d) Outline the different basic logic gates [3 marks]
- e) Utilizing boolean algebra, solve the following boolean expression  
 $F = C(B + C)(A + B + C)$  [5 marks]
- f) Differentiate between a latch and a flip flop. [2 marks]
- g) Distinguish between Minterms and Maxterms [2 marks]
- h) List the main categories of sequential circuits. [3 marks]

**QUESTION TWO [18 MARKS]**

- a) Define the term universal gates [2 marks]
- b) List the universal gates [2 marks]
- c) Draw a NOR gate and its truth table [3 marks]
- d) Outline the De Morgan's theorems hence prove them using truth table method. [6 marks]  
 $(\overline{A\overline{B}}) = \overline{A} + \overline{B}$
- e) Apply De Morgan's theorem to equate  $A(B + C)$  [2 marks]  
Create a logic circuit using NAND gates only for the expression  
 $X = A(B + C)$  [3 marks]

**QUESTION THREE [18 MARKS]**

- a) What is a shift register? [2 marks]
- b) Outline the basic types of registers [4 marks]
- c) State three applications of shift registers [3 marks]
- d) List the different types of counters and briefly explain how each of them works [9 marks]

**QUESTION FOUR [18 MARKS]**

- a) Contrast between combinational logic circuits and sequential logic circuits clearly stating all the differences with respect to their output, memory and fundamental building block **[6 marks]**
- b) Design a JK flip flop using a D flip flop **[12 marks]**

**QUESTION FIVE [18 MARKS]**

- a) With the help of a diagram, explain hence illustrate what you understand by the term “Don’t care terms”. **[4 marks]**
- b) State five main reasons for simplifying Boolean functions. **[5 marks]**
- c) Contrast between a standard Sum Of Products (SOP) and a standard
- d) (i) What is the function of a Karnaugh map. **[2 marks]**  
(ii) State the various kinds of Karnaugh maps **[3 marks]**
- Outline two different techniques used for simplifying boolean equations **[2 marks]**