

(Knowledge for Development)

KIBABII UNIVERSITY
UNIVERSITY EXAMINATIONS
2019/2020 ACADEMIC YEAR
SPECIAL/SUPPLEMENTARY EXAMINATION
YEAR ONE SEMESTER ONE EXAMINATIONS
FOR THE BACHELORS DEGREE
COMPUTER SCIENCE

COURSE CODE: CSC 113

COURSE TITLE: ELECTRONICS

DATE: 12/02/2021

TIME: 11.00 A.M – 01.00 P.M

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTION ONE AND ANY OTHER TWO (2) QUESTIONS

QUESTION ONE [COMPUSORY] [30 MARKS]

- a) Differentiate between
- i) intrinsic and extrinsic semiconductors (2 marks)
 - ii) p-type and n-type semiconductors (2 marks)
 - iii) donor and acceptor atoms (2 marks)
- b) With the aid of a labeled diagram explain the conduction of current in a good conductor. Why does a conductor have low resistance? (4 marks)
- c) Explain the following terms;
- (i) Positive feedback. (2marks)
 - (ii) Negative feedback. (2marks)
- d) With the aid of diagrams, illustrate four types of feedback. (2marks)
- e) Give a brief explanation on how a bipolar junction transistor amplifies current. (2 marks)
- f) What is the difference in the output when a single phase half-rectifier is replaced by a full-wave rectifier? (4 marks)
- g) Draw the schematic of a pn-junction diode in
- (i) Forward-biased mode. (3 marks)
 - (ii) reverse-biased mode (3 marks)
- Show in each case the polarity of voltage source (positive and negative terminal of the source) and the current direction.
- h) Determine the range of V for obtaining a regulated voltage shown in Fig.1(c) for the data
- $0 \leq I_L \leq 4mA$
 - $2 \leq I_Z \leq 8mA$
- (4 Marks)


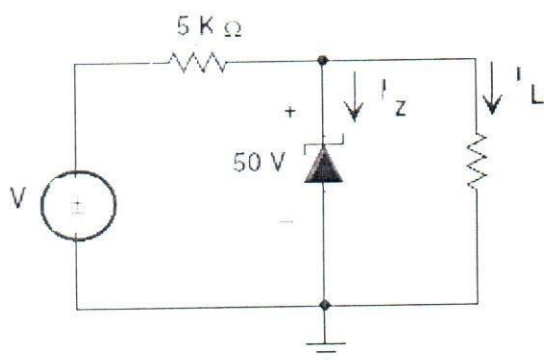


Figure 1(c)

QUESTION TWO [20 MARKS]

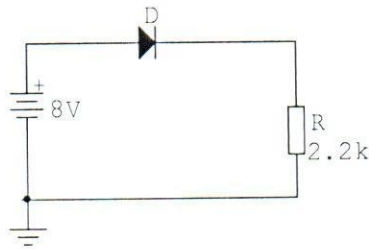- a) Explain the main difference between rectifier diode, light emitting diode and Zener diode. (3 marks)
- b) Describe Zener diode and briefly explain how it regulates the voltage? What happens to the series current, load current and Zener current when the d.c. input voltage of a Zener regulator increases? (7 marks)
- c) (i) For the series circuit shown determine V_D , V_R , and I_D . (3 marks)



- d) Derive the relation : $\alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}}$ (4 marks)

QUESTION THREE [20 MARKS]

- a) Explain the term “doping” and briefly explain why it is done in semiconductors (3 marks)
- b) A load line intersects the forward V-I characteristic of a silicon diode at Q, where the slope of the curve is 40mA/V. Calculate the diode resistance at the point Q. (4 marks)
- c) For the circuit shown in figure 3(a), draw the waveform of output voltage V_o . Assume ideal diode D and lossless capacitor C. (6 marks)

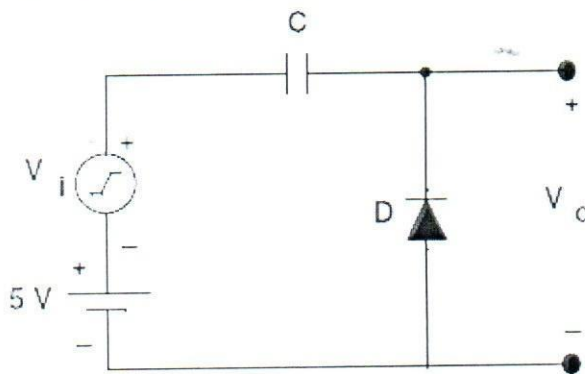


Figure 3(a)

- d) Describe the phenomenon of avalanche and zener breakdown. (4 marks)
- e) Explain physically how a p-n junction functions as a rectifier. (3 marks)

QUESTION FOUR [20 MARKS]

- a) Explain why a semiconductor behaves like an insulator at absolute zero temperature. (2 marks)
- b) Explain what happens to the conductivity of semiconductor with respect with rise in temperature. Compare with conductivity of metals. (3 marks)
- c) Explain the effect of temperature on extrinsic semiconductors (2 marks)
- d) Explain the effect of negative feedback on the following in amplifier;
- (i) Stability of amplifier again
 - (ii) Bandwidth (6 marks)
- e) Explain briefly how n- type and p- type materials are formed. (4 marks)
- f) Compare CB and CE transistor configurations with regard to AC input and output resistance. (3 marks)

QUESTION FIVE [20 MARKS]

- a) What is the importance of a valence shell and valence electrons? (3 marks)
- b) (i) Using transistor current relationship, derive the relationship between α , γ and β (4 marks)
- (ii) Briefly describe three modes of connection of a transistor in a circuit. (3 marks)
- (iii) Explain how a transistor is biased for amplification. (2 marks)
- c) For the Zener shunt regulator of figure 4(b), determine the load current, minimum and maximum Zener current. (8 marks)

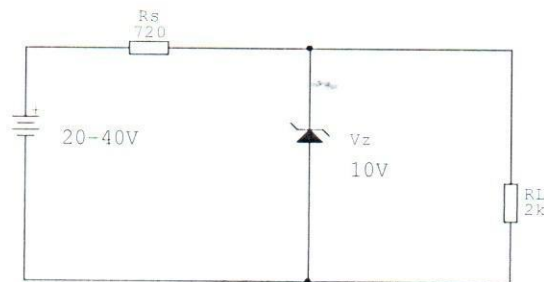


Figure 4b