



Handwritten signature or initials in red ink.

**KIBABII UNIVERSITY  
(KIBU)**

**UNIVERSITY EXAMINATIONS  
2020/2021 ACADEMIC YEAR**

**THIRD YEAR SECOND SEMESTER MAIN EXAMINATIONS**

**FOR THE DEGREE  
OF  
BACHELOR OF EDUCATION (SCIENCE)**

**COURSE CODE: SPH 327**

**COURSE TITLE: ELECTRONICS**

TIME: 2 Hours

**DATE: 5/10/2021**

**TIME: 2:00-4:00PM**

---

**INSTRUCTIONS TO CANDIDATES**

**Answer question ONE and any TWO of the remaining.**

**Symbols used bear the usual meaning.**


KIBU observes ZERO tolerance to examination cheating

This Paper Consists of 3 Printed Pages. Please Turn Over.

Useful constants  $V_{BE} = 0.7V$

### QUESTION ONE (30 MARKS)

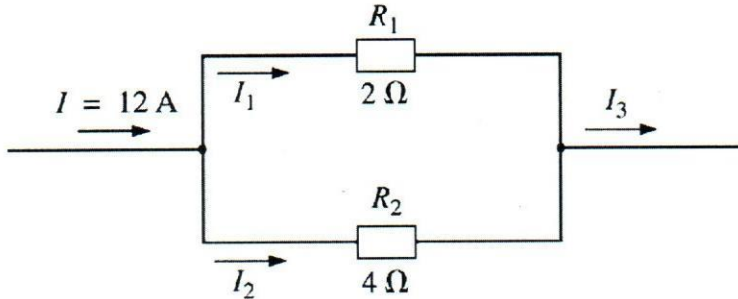
- a) With examples, distinguish between active and passive devices (2 marks)  
b) Define the following terms (i) branch (ii) node and (iii) loop (3 marks)  
d) State Kirchoff's laws. (2marks)  
c) Use current divider rule to determine  $I_1$  and  $I_2$  in the following circuit. (2 marks)



- d) Define doping? (1 marks)  
e) Use band gap theory to explain the difference between conductors, insulators and semiconductors. (6 marks)  
f) Explain the working principle of Zener diode. Draw its characteristics. (4 marks)  
g) Define energy bands, electrons and holes as used in semiconductor physics (3marks)  
g) Derive the relationship between  $\alpha$  and  $\beta$  giving their respective meaning. (2 marks)  
h) Draw a n-p-n transistor connected in Common emitter configuration showing clearly all the current directions. (3 marks)  
i) Differentiate between intrinsic and extrinsic semiconductors (2 mark)


### QUESTION TWO (20 MARKS)

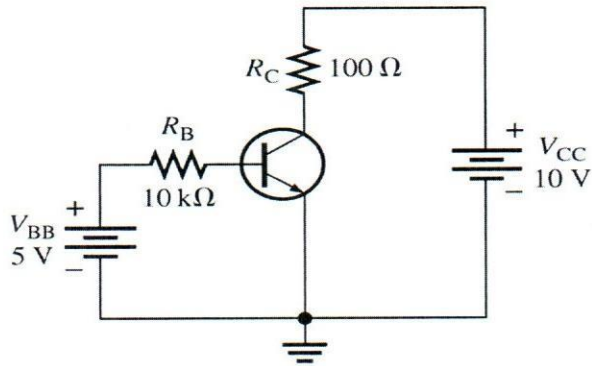- a) State and explain the function and application of diode clipper using a suitable diagram. (6 marks)  
b) Determine  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{CE}$  and  $V_{CB}$  in the circuit below. The transistor has a  $\beta = 150$ . (8 marks)



(c) Use Norton's theorem to find short  $AB$  and  $R_N = R_{TH}$ .


(6 marks)

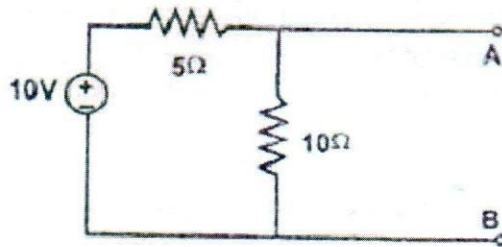

### QUESTION THREE (20 MARKS)

a) Use Mesh Current Analysis to find  $I_1$  and  $I_2$  in the following circuit

(7 marks)

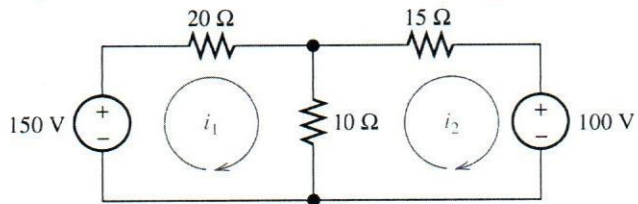


b) Describe how to obtain the input and output characteristics of common emitter npn transistor (Use a clear circuit diagram to illustrate your answer). (5 marks)

c) For a transistor connected in common emitter configuration, sketch the typical output characteristics relating collector current and the collector-emitter voltage, for various values of base current. Explain the shape of the characteristics. (8 marks)


### QUESTION FOUR (20 MARKS)

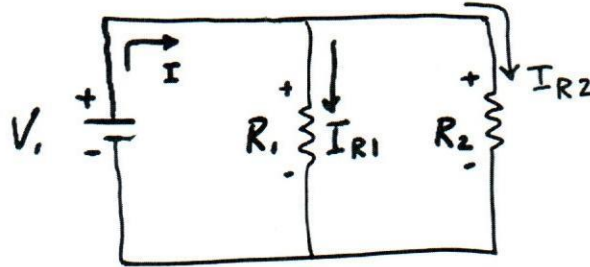a) Consider the circuit shown, where  $R_1 = 20\Omega$ ,  $R_2 = 40\Omega$ ,  $V_1 = 20V$ . Calculate (a) The current through  $R_1$ . (b) The current through  $R_2$ . (c) The current leaving the voltage source. (6 marks)




b) Briefly explain with a suitable diagram how D.C load line can be determined from a BJT characteristic curve. (7 marks)

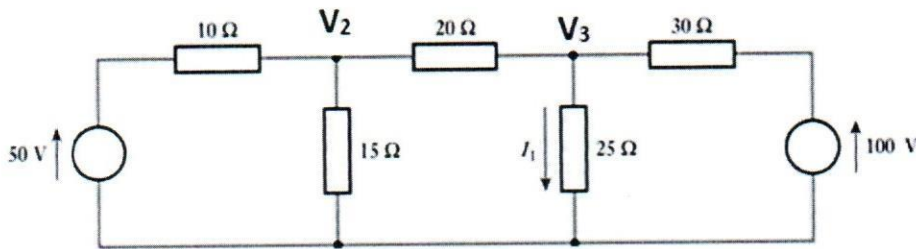c) c) Use Nodal analysis to determine the current  $I_1$  in the following circuit. (7 marks)



**QUESTION FIVE (20 MARKS)**

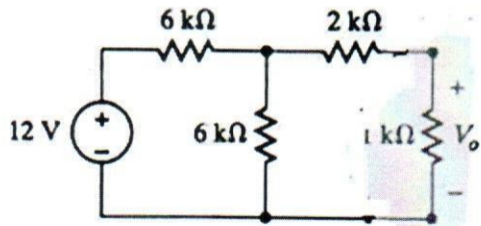- a) Describe the operation of PN junction diode under forward and reverse bias. (4 marks)
- b) Describe experiments to determine transistor characteristics (2marks)
- c) Explain applications of diodes and transistors (2marks)
- d) Using Thevenin's Theorem, determine  $V_o$  across parts A and B. (6 marks)



e) Explain clearly with suitable waveforms, the working of a half wave rectifier.

(6 marks)