



(Knowledge for Development)

KIBABII UNIVERSITY

**UNIVERSITY EXAMINATIONS
2017/2018 ACADEMIC YEAR**

**SUPPLEMENTARIES/SPECIAL EXAMINATIONS
YEAR ONE SEMESTER TWO EXAMINATIONS**

**FOR THE DEGREE OF
BACHELOR OF INFORMATION TECHNOLOGY**

COURSE CODE : BIT 124
COURSE TITLE : DIGITAL ELECTRONICS


DATE: 17/10/2018 **TIME: 8.00A.M. – 10.00A.M.**

INSTRUCTIONS TO CANDIDATES

ANSWER QUESTIONS ONE AND ANY OTHER TWO.

QUESTION ONE-COMPULSORY (30marks)

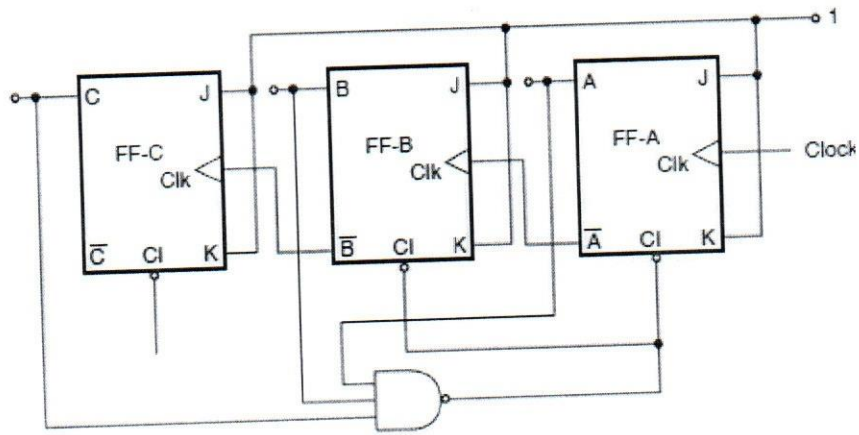
- a) Distinguish between Multiplexers and demultiplexers [1 mark]
- b) Convert the binary number $1010\ 1011.01111_2$ to;
 - i) Hexadecimal [2 marks]
 - ii) Decimal [2 marks]
- c) Convert hexadecimal number $A25C.2A$ to;
 - i) Binary [2 marks]
 - ii) Octal [2 marks]
- d) Refer to the counter schematic shown in the figure below.



- i) Sketch t [3 marks]
- ii) Determine the count sequence of this counter [2 marks]
- e) Determine SOP expression from the Karnaugh map shown below [3 marks]

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1		1
$\bar{A}B$		1		
AB				
$A\bar{B}$	1	1		1

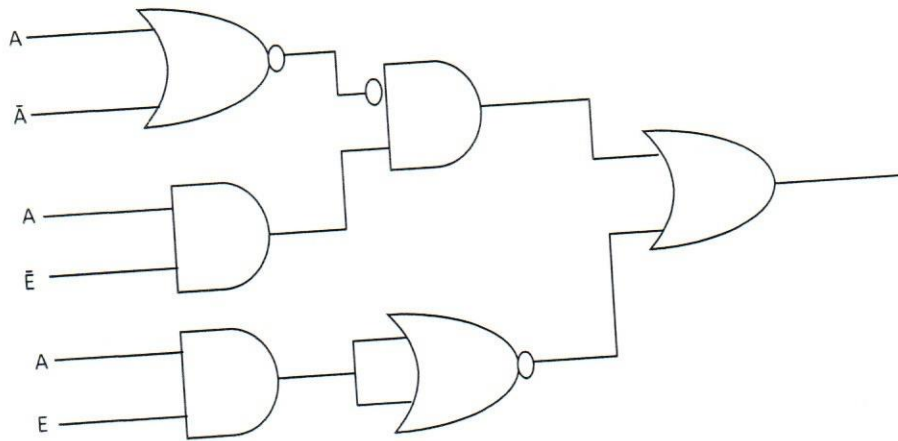- f) Determine the Boolean expression from the logic circuit shown below [3 marks]



- g) Simplify the following Boolean function obtained in (f) above to a minimum number of literals [3 marks]
- h) Obtain a truth table for the minimized logic circuit in 1(g) above [3 marks]
- i) Explain the application of magnitude comparator [4 marks]

QUESTION TWO

- a) Describe the operation of a decoder [6 marks]
- b) Using a logic circuit, illustrate how a comparator is used in testing of equality [3marks]
- c) Explain the operation of half- adder circuit as an arithmetic circuit [6 marks]
- d) Using relevant circuit diagram demonstrate synchronous parallel transfer of data from three bit register to another using J-K flip flops. [4 marks]

QUESTION THREE

- a) Design a digital logic circuit to produce a 50 Hz output signal from an input signal of 3.2 KHz. [4 marks]
- b) With the help of clocked JK flip flops and waveforms, explain the working of a MOD-8 down counter [5 marks]
- c) List any three applications of de-multiplexers [3 marks]
- d) Explain the operation of a decoder circuit [4 marks]
- e) Explain how a decoder is used in the following areas
- i) Computer memory [2 marks]
 - ii) Input/Output device addressing [2 marks]

QUESTION FOUR

- a) Explain any two applications for each of the following electronic circuit components
- i) Capacitors [2 marks]
 - ii) Diodes [2 marks]
- b) Using appropriate logic circuit diagram design a MOD 6 counter [5 marks]
- c) use the truth table below to answer questions (i)-(iii)

A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

- i) Write down the unsimplified Boolean expression [3 marks]
- ii) Use a Karnaugh map to minimize the Boolean expression [3 marks]
- iii) Implement the circuit from the minimized expression [2 marks]

QUESTION FIVE

- a) Briefly describe the operation of a Multiplexer [4 marks]
- b) Using appropriate logic circuit diagram design a MOD 6 counter [5 marks]
- c) The control circuit of a photocopier has four switches (A,B,C and D) placed along the path to detect a paper jam. Each switch is a normally open and as a paper passes over it, the switch closes. It is impossible for switch A and D to close at the same time
- The control circuit produces a HIGH output whenever two or more switches are closed at the same time to indicate a paper jam. The HIGH output sounds an alarm to alert the operator.
- i) Draw the truth table that satisfies the condition for sounding the alarm [3 marks]
- ii) Draw a karnaugh map from the results of the truth table [3 marks]
- iii) Obtain the switching formula from the K-map [3 marks]
- iv) Implement the circuit by using only NAND gates [2 marks]