

18



KIBABII UNIVERSITY

UNIVERSITY EXAMINATIONS
2019/2020 ACADEMIC YEAR

SECOND YEAR FIRST SEMESTER
SPECIAL/SUPP EXAMINATIONS

FOR THE DEGREE OF BSC RENEWABLE ENERGY AND BIOFUELS

COURSE CODE: REN 213

COURSE TITLE: BASIC ELECTRICAL TECHNOLOGY

DURATION: 2 HOURS

DATE: TIME: 01/02/21 11:00 - 1:00 PM

INSTRUCTIONS TO CANDIDATES

- Answer **QUESTION ONE** (Compulsory) and any other two (2) Questions.
- Indicate **answered questions** on the front cover.
- Start every question on a new page and make sure question's number is written on each page.

This paper consists of 4 printed pages. Please Turn Over



KIBU observes ZERO tolerance to examination cheating

Question One.

- a) Define the following terms
i) Valence electrons
ii) Positive charge fixed ion
iii) Doping (3 marks)
- a) i) Define the term Karnaugh maps as used in Boolean algebra (1 marks)
- ii) Simplify the Boolean logic expression
$$A = x.y + \bar{y}.z + x.z + x.y.z$$
 (4 marks)
- b) With a well labeled diagram and transfer characteristics describe the construction an n-channel JFET (4 marks)
- c) i) What value of series resistor is required to limit the current through a LED to 20 mA with a forward voltage drop of 1.6 V when connected to a 10V supply? (3 marks)
- ii) With aid of necessary diagrams explain the operation of a Varactor diode (4 marks)
- d) State FOUR conditions to be met by transistor so that it acts as faithful amplifier (4 marks)
- e) Describe the operation of common base amplifier transistor configuration (4 marks)
- f) Define the following terms as applied in filter circuits (3 marks)
i) Low pass filter
ii) High pass filter
iii) Band pass filter

Question Two

- a) Define the following terms
i) Combinational logic circuit
ii) Sequential logic circuit (2 marks)
- b) Draw a well labeled diagram and explain using clock pulses the working principle of S-R flip flop (6 marks)
- c) Draw the circuit diagram of twisted ring counter and explain its operation (4 marks)
- d) Simplify the following expression
$$Y = (a.b.(c + \bar{b}.d) + \bar{a}.b).c.d$$
 (4 marks)
- e) With aid of circuit diagram and truth table describe the operation of **full adder** (4 marks)

Question Three.

- a) Define the following terms as applied in transistor amplifiers
- Emitter efficiency (γ)
 - Transport factor (β^*)
 - Large signal current gain (α)
- (3 marks)
- b) With aid of a suitable diagram describe the construction of an n-type semiconductor
(3 marks)

- c) Show that the stability factor of a transistor is given by the expression

$$S = \frac{1 + \beta}{1 - \beta \frac{dI_B}{dI_C}} \quad (4 \text{ marks})$$

- d) With aid of a circuit diagram describe the principle of operation of emitter feedback bias mode of transistor biasing
(4 marks)

- e) The fig 1 shows silicon BJT transistor voltage divider biasing circuit, if $R_1=2k\Omega, R_2=4k\Omega, R_E=1k\Omega, V_{CC}=12V$ and $\beta=50$. Calculate the following parameters
- Base current (I_B)
 - Collector current (I_C)
- (6 marks)

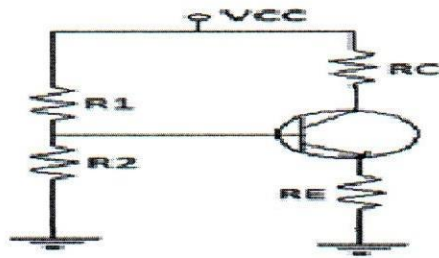


Fig 1

Question Four.

- a) i) State THREE advantages of FETs over BJT transistors
(3 marks)
- b) Explain the following terms as applied in FETs
- Ohmic region
 - Cut off region
 - Saturation region
 - Break down region
- (4 marks)
- c) With a well labeled diagram and transconductance curve describe the construction and operation of n-channel MOSFET in the depletion mode
(6 marks)

- d) State THREE advantages of using LEDs over incandescent lamps (3 marks)
- e) With suitable diagrams explain the principle of operation of tunnel diode (4 marks)

Question Five.

- a) The input and output voltages of a filter network are 16 mV and 8 mV respectively. Calculate the decibel level of the output voltage (3 marks)
- b) i) With aid of circuit diagram and waveforms describe the operation of a low pass filter (4 marks)
- c) A Low Pass Filter circuit consisting of a resistor of $4k7\Omega$ in series with a capacitor of $47nF$ is connected across a 10V sinusoidal supply. Calculate the output voltage (VOUT) at a frequency of 100Hz (3 marks)
- d) Design a high-pass RL filter that has a cutoff frequency of 4 kHz when $R = 3 k\Omega$. It is connected to a $10\angle 0^\circ$ V variable frequency supply. Calculate the output voltage V_0 and its decibel decrease at
- (i) $f = 0$
 - (ii) $f = f_c$
 - (iii) $f = 8$ kHz (6 marks)
- e) State FOUR functions of a microprocessor (4 marks)