

*(Handwritten signature)*



*(KNOWLEDGE FOR DEVELOPMENT)*

**KIBABII UNIVERSITY**

**UNIVERSITY EXAMINATIONS**

**2019/2020 ACADEMIC YEAR**

**SPECIAL/SUPPLEMENTARY EXAMINATIONS**

**YEAR ONE SEMESTER TWO EXAMINATIONS**

**FOR THE BACHELORS OF SCIENCE IN  
COMPUTER SCIENCE**

**COURSE CODE: CSC 122**

**COURSE TITLE: DIGITAL ELECTRONICS I**

**DATE: 01/02/2021 TIME: 2.00 P.M – 4.00 P.M**

**INSTRUCTIONS TO CANDIDATES**

**ANSWER QUESTION ONE AND ANY OTHER TWO (2) QUESTIONS**

**QUESTION ONE [COMPUSORY] [30MARKS]**

- a) Explain what is meant by radix (or base) of a number system. [2 Marks]
- b) Explain what is meant by LSB and MSB as used with number systems. [2 Marks]
- c) The diagram below shows the symbol for one type of logic gate.



- i) Name the logic gate [1 Mark]
- ii) Draw the truth table for this logic gate. [3 Marks]
- d) Simplify the following Boolean expressions using De Morgan's theorem and/or Boolean algebra

$$\overline{ABC} + BC + \overline{AC} \quad \text{[6 Marks]}$$

- e) Copy and complete the truth table for each of the logic gate [6 Marks]

Inputs		Truth Table Outputs for 2-input Logic Gates					
B	A	AND	NAND	OR	NOR	EX-OR	EX-NOR
0	0						
0	1						
1	0						
1	1						

- i) Complete the output column Q in the truth table for this logic circuit[4Marks]

A	B	S	Q
0	0	0	
0	1	0	
1	0	0	
1	1	0	
0	0	1	
0	1	1	
1	0	1	
1	1	1	

- f) Convert the following expression to standard sum-of-products form [2 Marks]

$$F = B + B[AC + (B + \overline{C})A]$$

- g) Simplify the following Boolean equation, in sum-of-products form, using Karnaugh map. Give the logic implementation of the simplified function in SOP form using suitable gates.


$$f = ABC\overline{D} + \overline{B}C\overline{D} + \overline{A}BCD + ABD + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}C\overline{D} \quad \text{[8 Marks]}$$

**QUESTION TWO [20MARKS]**

- a) Using NAND gates only show how the following gates are obtained [5 Marks]
- (i) NOT
  - (ii) OR
  - (iii) AND
- b) 0, 1, 3 and X are the independent digits/symbols of an arbitrary number system. What is the radix/base of this number system? List the first 16 numbers in this number system. [4Marks]
- c) For the logic expression  $Z = \overline{AB} + \overline{AB}$
- i) Obtain the truth table. [3Marks]
  - ii) Realize this operation using AND, OR, NOT gates [4Marks]
  - iii) Implement using only NAND gates [4Marks]

**QUESTION THREE [20 MARKS]**

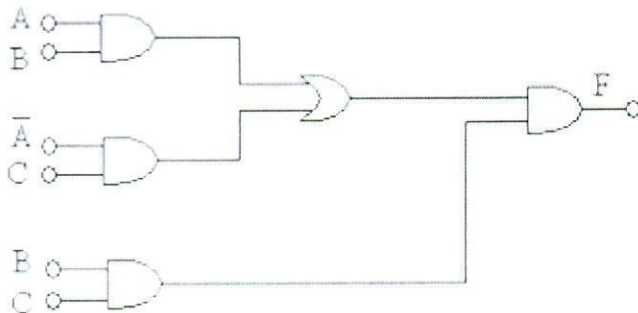- a) Consider the logic circuit below. Prepare the truth table for the output 'F' and write the standard SOP expression for F. [10Marks]



- b) Find the octal equivalent of  $(73.75)_{10}$  [6Marks]
- c) Map the standard SOP expression onto K-map [4Marks]
- $$ABC\overline{D} + \overline{A}BC\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D}$$

**QUESTION FOUR [20 MARKS]**

- a) For the function below, draw its truth-table hence minimize the function using K-map. Draw the logic diagram using gates of your choice to realize the minimized function.

$$f(A, B, C) = A\overline{B}\overline{C} + ABC + \overline{A}BC \quad [10Marks]$$

- b) Simplify the following Boolean equation, in product-of- sum form; using Karnaugh map. [10Marks]
- $$f = \overline{A}B + ABC\overline{D} + BC + \overline{A}B\overline{D}$$

**QUESTION FIVE [20 MARKS]**

- a) Convert  $57.4801_{10}$  to its binary equivalent to 14-bit accuracy. [6Marks]
- b) Simplify the following expression using Boolean algebra technique [4Marks]
- $$Z = AB + A(B + C) + B(B + C)$$



c) Using the truth table 1 below

i) Write the Boolean expression

ii) Transfer the input-output specification given for F to 3 variable Karnaugh map

iii) Draw the logic circuit represented by the simplified expression using AND, NOT and OR gates. [10mks]

Table 1: Truth table

Inputs			Output
A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0