

(Knowledge for Development)

KIBABII UNIVERSITY

**UNIVERSITY EXAMINATIONS
2019/2020 ACADEMIC YEAR**

**END OF SEMESTER EXAMINATIONS
YEAR TWO SEMESTER ONE EXAMINATIONS**

**FOR THE DEGREE OF
BACHELOR OF SCIENCE COMPUTER SCIENCE**

COURSE CODE: CSC 211

COURSE TITLE: DIGITAL ELECTRONICS II

DATE: 05/02/2021 TIME: 02.00 P.M - 04.00P.M

INSTRUCTIONS TO CANDIDATES


ANSWER QUESTIONS ONE AND ANY OTHER TWO.

QUESTION ONE [COMPULSORY] [30 MARKS]

a) (i) What is a full adder

(1mark)

 (ii) The logic diagram of Fig. 1 performs the function of a very common arithmetic building block. Identify the logic function. **(4 marks)**



b) Draw a 4-1 multiplexer circuit diagram and derive its truth table

(5 marks)

c) Outline any five applications of flip flops

(5 marks)

d) (i) Mention any three types of D/A converters

(3 marks)

(ii) An eight-bit D/A converter has a step size of 20 mV. Determine the full-scale output and percentage resolution. **(6 marks)**

e) (i) What is a microprocessor

(1mark)

(ii) List of any five desirable characteristics of a microprocessor

(5 marks)


QUESTION TWO [20 MARKS]

a) Distinguish between asynchronous and synchronous systems

(2 marks)

b) Draw a well-labelled diagram of a clocked RS flip-flop using NAND gates. Derive its truth table (3 marks)

 c) Given the timing diagram in Figure below, write out the truth table for the circuit responsible for it, the Boolean equation describing its operation and draw the actual circuit. (12 marks)



QUESTION THREE [20 MARKS]

a) Distinguish between a multiplexer and an encoder

(2 marks)


b) A 3-bit binary number is represented as $A_2 A_1 A_0$, where A_0 is the LSB. Design a logic circuit which will produce a HIGH output whenever the binary number is either 1, 2, 4 or 7. Implement the circuit using a 1 to 4 MUX. (3 marks)

c) Show how gated-SR flip-flop can be modified to operate as a D flip-flop and draw the truth table for D flip-flop. (7 marks)

d) Write out the truth table for the 4-line-to-2-line encoder that takes a four-line decimal signal and converts it to binary code. Design and draw the circuit to implement this encoder. (8 marks)

QUESTION FOUR [20 MARKS]

 - a) Determine the size of the PROM required for implementing the following logic circuits:
- (i) a binary multiplier that multiplies two four-bit numbers; (2 marks)
 - (ii) a dual 8-to-1 multiplexer with common selection inputs; (2 marks)
 - (iii) a single-digit BCD adder/subtractor with a control input for selection of operation. (4 marks)
- b) Design a mod-10 binary up-counter using negative edge JK flip-flops with active-LOW clear. (8 marks)
- c) Fig.2 below shows the internal logic circuit diagram of one of the four D latches of a four-bit D-latch in IC 7475.
- (i) Give an argument to prove that the Q output will track the D input only when the ENABLE input is HIGH. (2 marks)
 - (ii) Prove that the Q output holds the value it had just before the ENABLE input went LOW during the time the ENABLE input is LOW. (2 marks)



QUESTION FIVE [20 MARKS]

- a) Briefly explain the desirable characteristics of a digital to analogue converter (DAC) (6 marks)
- b) Using a well-labelled schematic diagram, explain how a weighted binary resistance summing amplifier functions as a digital-to-analog converter (DAC). (9 marks)
- c) State any five applications of D/A converters (5 marks)