



(Knowledge for Development)

KIBABII UNIVERSITY
(KIBU)

UNIVERSITY EXAMINATIONS
2021/2022 ACADEMIC YEAR

END OF SEMESTER EXAMINATIONS
YEAR TWO SEMESTER TWO EXAMINATIONS

FOR THE DIPLOMA
(INFORMATION TECHNOLOGY)

COURSE CODE : **DIT 079**
COURSE TITLE : **DIGITAL ELECTRONICS**

DATE: 01/09/2022 **TIME: 9.00 A.M.-10.00 A.M.**

INSTRUCTIONS TO CANDIDATES
ANSWER QUESTIONS ONE AND ANY OTHER TWO.

QUESTION ONE (COMPULSORY) [24 MARKS]

- a. Categorize the different ways of representing numerical values of quantities. [2 marks]
- b. Define the term digital quantity hence state an example. [3 marks]
- c. Name the different number systems used in digital technology. [4 marks]
- d. Outline the different basic logic gates [3 marks]
- e. Utilizing boolean algebra, solve the following boolean expression
- $$F = C (B + C) (A + B + C)$$
- [5 marks]
- f. Differentiate between a latch and a flip flop. [2 marks]
- g. Distinguish between Minterms and Maxterms [2 marks]
- h. List the main categories of sequential circuits. [3 marks]

QUESTION TWO [18 MARKS]

- a. Define the term universal gates [2 marks]
- b. List the two universal gates [2 marks]
- c. Draw a NOR gate and its truth table [3 marks]
- d. Outline the De Morgan's theorems hence prove them using truth table method. [6 marks]
- e. Apply De Morgan's theorem to equate $A(B + C)$ [2 marks]
- f. Create a logic circuit using NAND gates only for the expression
- $$X = A (B + C)$$
- [3 marks]

QUESTION THREE [18 MARKS]

- a. What is a shift register? [2 marks]
- b. Outline the basic types of registers [4 marks]
- c. State three applications of shift registers [3 marks]
- d. List the different types of counters and briefly explain how each of them works [9 marks]

QUESTION FOUR [18 MARKS]

- a. Contrast between combinational logic circuits and sequential logic circuits clearly stating all the differences with respect to their output, memory and fundamental building block [6 marks]
- b. Design a JK flip flop using a D flip flop [12 marks]

QUESTION FIVE [18 MARKS]

- a. With the help of a diagram, explain hence illustrate what you understand by the term "Don't care terms". [4 marks]
- b. State five main reasons for simplifying Boolean functions. [5 marks]
- c. Contrast between a standard Sum Of Products (SOP) and a standard Product Of Sums with respect to digital electronics [2 marks]
- d. (i) What is the function of a Karnaugh map. [2 marks]
(ii) State the various kinds of Karnaugh maps [3 marks]
- e. Outline two different techniques used for simplifying boolean equations [2 marks]