



*(KNOWLEDGE FOR DEVELOPMENT)*

**KIBABII UNIVERSITY  
(KIBU)**

**UNIVERSITY EXAMINATIONS  
2020/2021 ACADEMIC YEAR**

**END OF SEMESTER EXAMINATIONS  
YEAR ONE SEMESTER ONE EXAMINATION**

**FOR THE DEGREE OF  
(INFORMATION TECHNOLOGY)**

**COURSE CODE: BIT 115**

**COURSE TITLE: BASIC ELECTRONICS**

**DATE: 27/01/2022      TIME: 2.00P.M- 4.00P.M**

---

**INSTRUCTIONS**

**ANSWER QUESTIONS ONE AND ANY OTHER TWO.**

**QUESTION ONE (COMPULSORY) [30 MARKS]**

- (a) List any two passive device and two active devices [4 marks]
- (b) Jane has three resistors of magnitude 200, 400 and 800 ohms. She has DC battery of 10 Volts. Determine [6 marks]
- (i) The current in circuit if she connects the three resistors in series
- (ii) The current in 800 ohms resistor if she connects the three parallel
- (c) Determine the parallel resonance frequency of 10 microFarad capacitor and 0.2Henries inductor [3 marks]
- (d) Distinguish between ; [10 marks]
- (i) Donor and acceptor semiconductor
- (ii) Semiconductor and Insulator
- (iii) Intrinsic and Extrinsic conduction in semiconductor
- (iv) A bipolar and unipolar transistors
- (v) Wide band and narrow band amplifies
- (e) Show that gain with feedback of an amplifier is given by  $A_{vf} = A_v / (1 + \beta A_v)$  [4 marks]
- (f) List the three configuration of amplifier [3 marks]

**QUESTION TWO [20 MARKS]**

- (a) With aid of circuit diagram of RC coupled amplifier explain the function of each components [10 marks]
- (b) With aid the frequency response diagram of the circuit in (a) above [10 marks]
- (i) Explain the response
- (ii) write an expression for bandwidth
- (iii) Explain how you increase the bandwidth and resulting trade off

**QUESTION THREE [20 MARKS]**

- (a) Explain the stages of operation amplifier [8 marks]
- (b) With aid of circuit diagram derive the transfer function of the following OPAM circuit
- (i) Inverting amplifier
- (ii) Integrator
- (iii) Summer [12 marks]

**QUESTION FOUR [20 MARKS]**

- (a) With the aid of circuit diagram and waveform of full wave bridge rectifier explain its operation [12marks]
- (b) For circuit in (a) above for 240 AC Volts is fed on the primary side of step-down transformer whose turn ratio 20:5. Determine [8 marks]
- (i) Voltage at secondary side
- (ii) DC output voltage

**QUESTION FIVE [20 MARKS]**

- (a) With aid of circuit diagram and waveforms explain the operation of tuned collector oscillator [10 marks]

- (b) With aid of diagram derive the expression for drawing [6 marks]
- (i) DC load line
  - (ii) AC load line
- (c) With aid of diagram and waveform illustrate class B operation of amplifier [ 4 marks]