



(Knowledge for Development)

KIBABII UNIVERSITY

**UNIVERSITY EXAMINATIONS
2020/2021 ACADEMIC YEAR**

**SPECIAL/SUPPLEMENTARY EXAMINATIONS
YEAR ONE SEMESTER TWO EXAMINATIONS**

**FOR THE DEGREE OF
BACHELOR OF INFORMATION TECHNOLOGY**

COURSE CODE : BIT 124

COURSE TITLE : DIGITAL ELECTRONICS

DATE: 01/10/2021 TIME: 11.00 A.M-1.00 P.M


INSTRUCTIONS TO CANDIDATES

ANSWER QUESTIONS ONE AND ANY OTHER TWO.

SECTION A

QUESTION ONE-COMPULSORY (30marks)

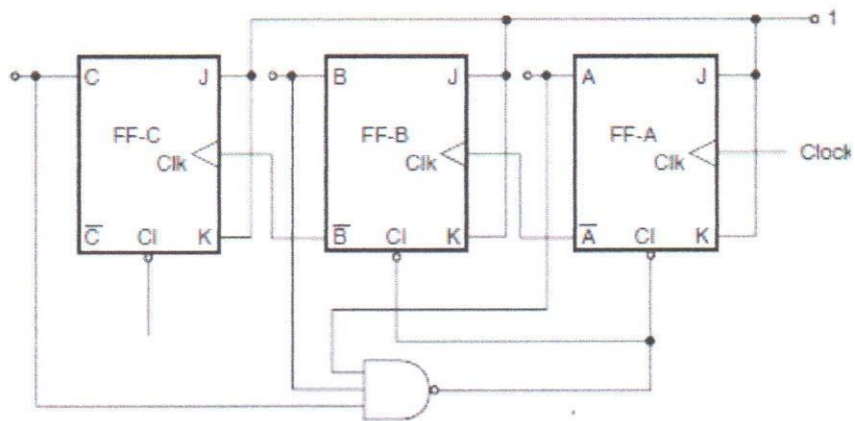
- a) Distinguish between Multiplexers and demultiplexers [1 mark]
- b) Convert the binary number $1010\ 1011.01111_2$ to;
 - i) Hexadecimal [2 marks]
 - ii) Decimal [2 marks]
- c) Convert hexadecimal number A25C. 2A to;
 - i) Binary [2 marks]
 - ii) Octal [2 marks]
- d) Refer to the counter schematic shown in the figure below.



- i) Sketch the wave forms for the output of the flipflops [3 marks]
 - ii) Determine the count sequence of this counter [2 marks]
- e) Determine SOP expression from the Karnaugh map shown below [3 marks]

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	1	1		1
$\overline{A}B$		1		
AB				
$A\overline{B}$	1	1		1

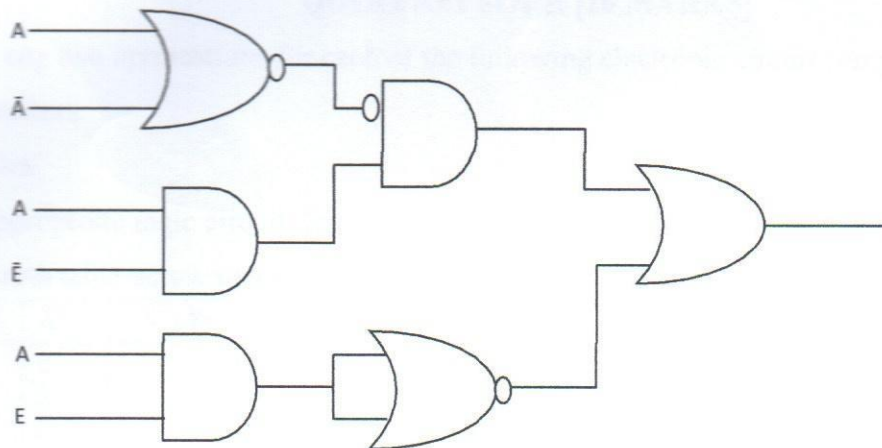- f) Determine the Boolean expression from the logic circuit shown below [3 marks]



- g) Simplify the following Boolean function obtained in (f) above to a minimum number of literals [3 marks]
- h) Obtain a truth table for the minimized logic circuit in 1(g) above [3 marks]
- i) Explain the application of magnitude comparator [4 marks]

QUESTION TWO [20 MARKS]

- a) Describe the operation of a decoder [6 marks]
- b) Using a logic circuit, illustrate how a comparator is used in testing of equality [3marks]
- c) Explain the operation of half- adder circuit as an arithmetic circuit [6 marks]
- d) Using relevant circuit diagram demonstrate synchronous parallel transfer of data from three bit register to another using J-K flip flops. [4 marks]

QUESTION THREE [20 MARKS]

- a) Design a digital logic circuit to produce a 50 Hz output signal from an input signal of 3.2 KHz. [4 marks]
- b) With the help of clocked JK flip flops and waveforms, explain the working of a MOD-8 down counter [5 marks]
- c) List any three applications of de-multiplexers [3 marks]
- d) Explain the operation of a decoder circuit [4 marks]
- e) Explain how a decoder is used in the following areas [2 marks]
- i) Computer memory

ii) Input/Output device addressing

[2 marks]

QUESTION FOUR [20 MARKS]

a) Explain any two applications for each of the following electronic circuit components

i) Capacitors

[2 marks]

ii) Diodes

[2 marks]

b) Using appropriate logic circuit diagram design a MOD 6 counter

[5 marks]

c) use the truth table below to answer questions (i)-(iii)

A	B	C	D	X
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

i) Write down the unsimplified Boolean expression

[3 marks]

ii) Use a Karnaugh map to minimize the Boolean expression

[3 marks]


iii) Implement the circuit from the minimized expression

[2 marks]

QUESTION FIVE [20 MARKS]

a) Derive a truth table for the circuit below.

[4 marks]

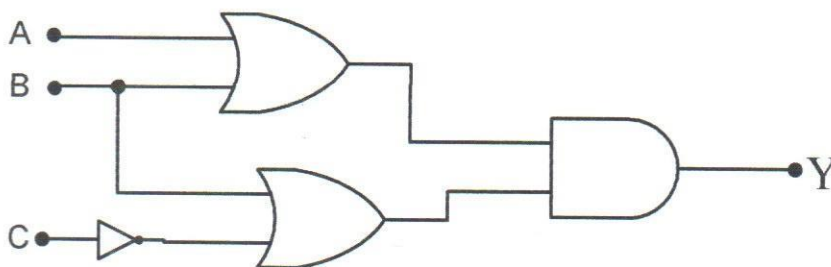

- b) Describe the operation of flip flops in frequency division circuits [6 marks]
- c) Explain any three applications of decoder circuits [6 marks]
- d) Differentiate between multiplexers and de-multiplexers [4 marks]

35