



KIBABII UNIVERSITY

**UNIVERSITY EXAMINATIONS
2022/2023 ACADEMIC YEAR**

**SECOND YEAR FIRST SEMESTER
MAIN EXAMINATIONS**

**FOR THE DEGREE OF B.SC (RENEWABLE ENERGY AND BIOFUELS
TECHNOLOGY)**

COURSE CODE: REN 213

COURSE TITLE: BASIC ELECTRONICS TECHNOLOGY

DATE: 19/12/2022

TIME: 2:00-4:00PM

INSTRUCTIONS TO CANDIDATES

TIME: 2 Hours

Answer question ONE and any TWO of the remaining

KIBU observes ZERO tolerance to examination cheating

Question One (Compulsory)

- a) Define the term 'doping' as used in semiconductors. (2 marks)
- b) What is meant by contact potential in a P-N junction? (3 marks)
- c) State two reasons for biasing a transistor (2 marks)
- d) State three main properties of an op-amp. (3 marks)
- e) Define common-mode rejection ratio of an op-amp. (2 marks)
- f) Define the following terms as used in filters. (5 marks)
 - i) Attenuation
 - ii) Cut-off frequency
 - iii) Propagation constant
 - iv) High pass filter
 - v) Band-stop filter
- g) Name any **THREE** types of number systems. (3 marks)
- h) Define a logic gate (2 marks)
- i) State **FOUR** types of logic gates. (4 marks)
- j) Briefly explain any **FOUR** types of flip-flops. (4 marks)

Question Two

- a) With aid of a diagram, describe the operation of a NPN bipolar junction transistor. (8 marks)
- b) With the aid of a labelled diagram, describe the formation of a p-type semiconductor. (2 marks)
- c) With the aid of a labelled construction diagram, describe the operation of an n-channel depletion MOSFET and sketch its output characteristic curves. (10 marks)

Question Three

- a) For the summing op-amp shown in figure 1, determine the output voltage, V_0 . (10 marks)

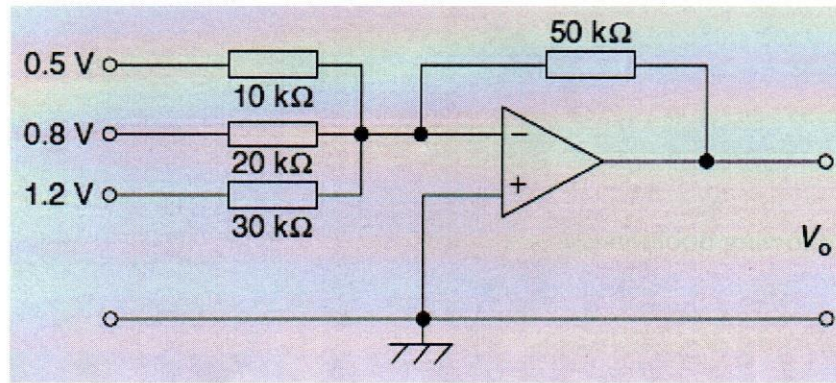


Figure 1

- b) Determine the cut-off frequency and the nominal impedance for the low-pass T-connected section shown in figure 2. (10 marks)

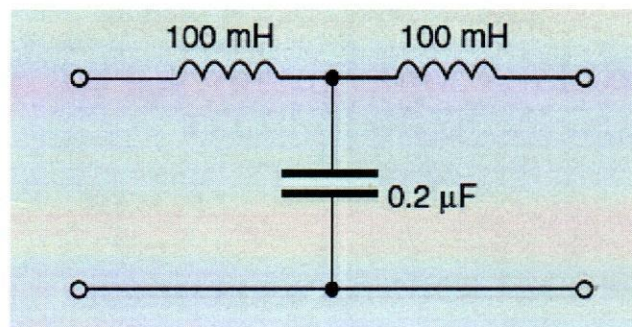


Figure 2

Question Four

- a) Convert 11001_2 to its equivalent decimal number. (6 marks)
- b) State **THREE** uses of octal number system. (3 marks)
- c) Figure 3 below shows a three input OR gate. Draw its truth table. (6 marks)

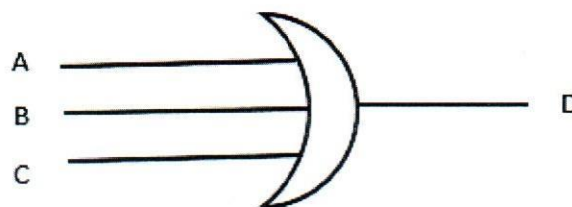


Figure 3

- d) List any **FIVE** applications of logic gates. (5 marks)

Question Five

- a) Simplify the following Boolean expression and draw the logic circuit for the simplified expression. (6 marks)

$$Y = \bar{A}BC + A\bar{B}C + ABC + B\bar{C}$$

- b) A Boolean expression is given by; (14 marks)

$$Y = \bar{A}BC + ABC + B\bar{C}D$$

- i) Obtain a truth table for the expression.
- ii) Simplify the expression using Karnaugh map.